

Inductive Adder Modulators for ILC DR Kickers

Craig Burkhart *SLAC*

For SLAC-LLNL Team

Ed Cook, C. Brooksby *LLNL*


R. Cassel, T. Beukers, C. Burkhart,
M. Nguyen, R. Larsen *SLAC*

September 26, 2006

Inductive Adder Modulators for ILC DR Kickers

- SLAC/LLNL Program
- Inductive Adder Topology
- Inductive Adder Modulators
- Areas of Advanced Development for ILC DR Applications

System Topology

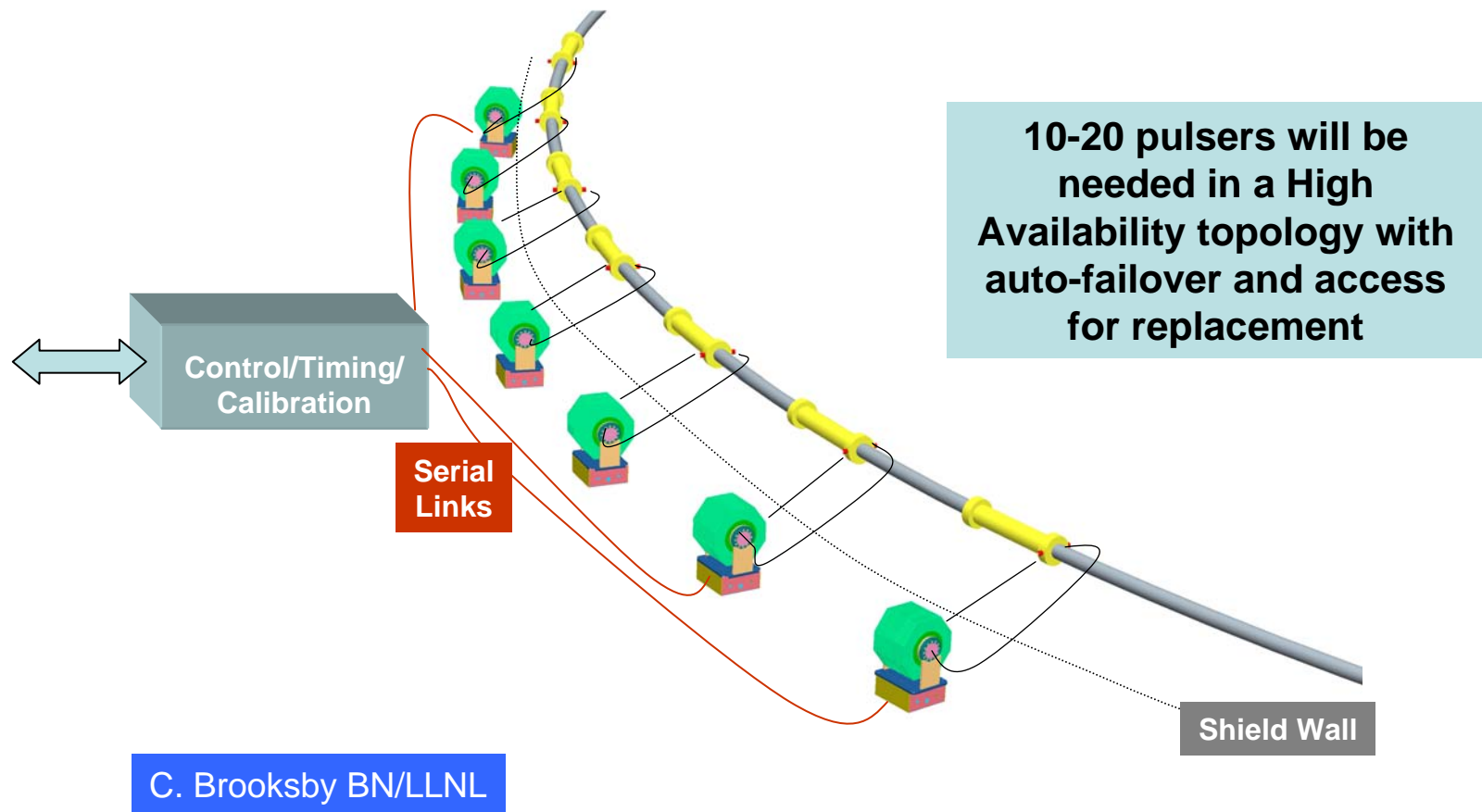

DR Kicker Modulator Requirements

Pulse Length:	~5 ns
Output Voltage:	± 10 kV (two simultaneous pulses of opposite polarity required)
Load Impedance:	50 Ω
Burst Repetition Rate:	~3MHz
Burst Duration:	~ 3000 Pulses
Average Repetition Rate:	15,000 PPS (5 bursts per second)
Intra-pulse Stability:	7×10^{-4}
Bunch spacing:	20 ns

SLAC/LLNL High Availability (HA) Damping Ring Kicker System Development Program

- Goal: Demonstrate *Full System Architecture* for HA Damping Ring Kicker System
 - Develop prototype
 - Multiple unit operation
 - System timing
 - Calibration
 - Diagnostics
 - Auto-failover
 - Demonstrate reliability
 - Evaluate System Trade-offs

SLAC/LLNL High Availability (HA) Damping Ring Kicker System Development Program

- Motivation
 - System Development: Many groups working on kickers to optimize pulse shape, but overall system needs prototype demonstration.
 - High Availability: Reliability/Availability critical for system of ~ 10-20 or more pulsers in series.
 - Inductive Adder: Induction modulator has ideal balanced output architecture (+/- 10kV output) but needs optimization for rise & fall time, impedance matching, stability of calibration, HA service features.

Basic Design

- Modular Inductive Adder Topology
 - Extra modules and auto-failover if one or two modules fail
 - Each module has multiple MOSFETs in parallel
 - Balanced output for identical pulses to each side of kicker e.g. 200A into 50 Ohms
 - Multiple units to make full kicker system
 - Small units easily substituted when one fails
 - Redundancy in form of extra kickers for >99% Availability
 - Sophisticated card-level diagnostics for HA management

FY '07 Goals


- Complete development and testing of short pulse (~ 5 ns) module
- Initiate development of prototype modulator: 5 ns, ± 10 kV, 50 Ω , 3 MHz
- Start design of calibration system
- Initiate design of timing system

SLAC/LLNL FY '07 Budget (pro-forma)

- **LLNL**
 - \$225k M&S (transfer from SLAC)
 - Fractional support: E. Cook, designer, & tech
 - Prototype development
- **SLAC**
 - 0.3 FTE
 - Prototype support systems development: controls, timing, & calibration

Inductive Adder Circuit Topology

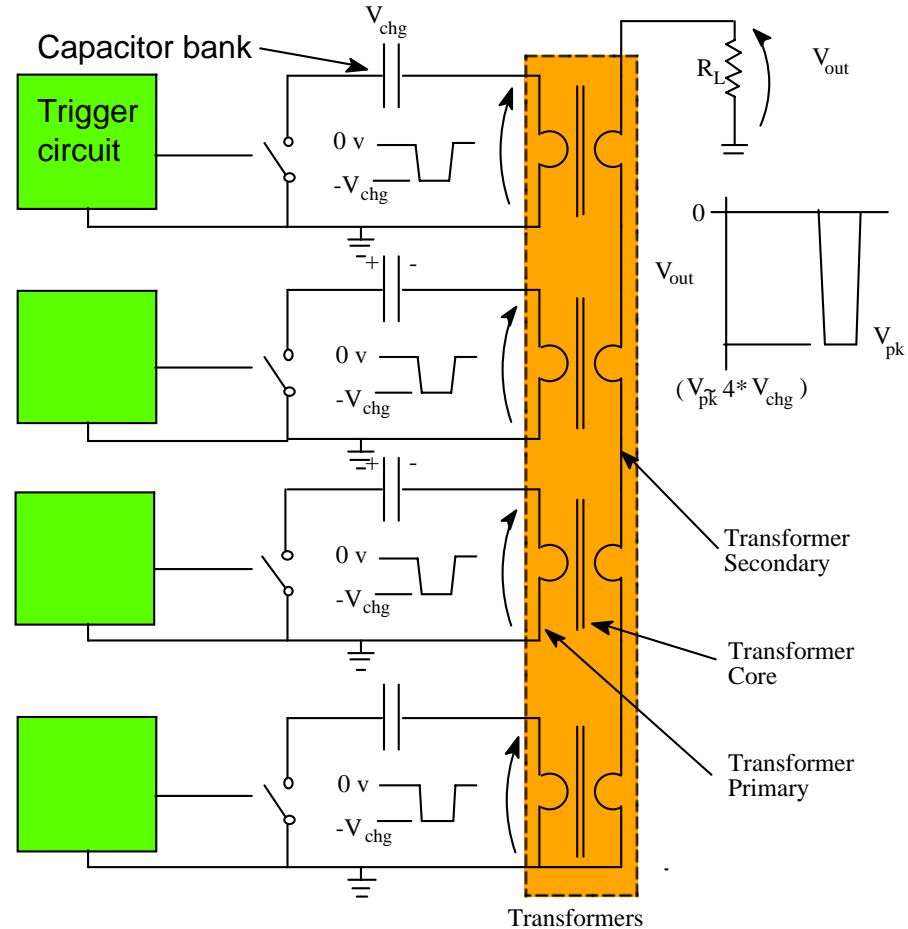Note:
Conceptually, for fast pulses, the mechanical structure of an inductive adder is virtually identical to that of an induction accelerator



Inductive Adder Concept - Simplified Schematic

E. Cook LLNL

Inductive Adder Topology: Advantages

- **Modular: Adder comprised of a stack of identical modules**
 - Topology arrays discrete switching devices: parallel/series
 - All modules triggered independently
 - Scalable to higher voltages by adding modules
 - Redundant: can run n/N
- **Single-turn transformer has high bandwidth**
- **All drive components ground referenced**
- **No dc high voltage**
- **Pulse format defined by external trigger generator**
 - Pulse width and PRF agility
 - High burst frequency: >1 MHz

LLNL Inductive Adder Systems


- Dual-Axis Radiographic Hydrodynamics Test Facility (LANL)
 - $\pm 18\text{kV} \pm 10\%$ into 50Ω
 - 10ns rise and fall times
 - 16–200ns adjustable pulse width
- Plasma Electrode Pockel Cell (LLE/LLNL)
 - 0-20kV into capacitive load ($Z \sim 12.5 \Omega$)
 - 0-200ns flattop to $\pm 1\%$
- Accelerator Test Facility (KEK)
 - $\pm 8.5\text{kV}$ into 50Ω
 - ~ 10 ns flattop, ~ 20 ns FWHM

$\pm 18\text{kV}$ Pulsers for DARHT Dipole Kicker




DARHT Modulator Output Characteristics


Output:
30 ns,
18 kV,
50 Ω

 

 
4-Pulse
Agile Burst:
Pulse Width
Frequency




Output:
120 ns,
20 kV,
50 Ω

 

 4-Pulse
Agile Burst:
Amplitude
Modulation




NIF PEPC Modulator


 


**Completed assembly
w/ temporary control
panel**

 **Controls, power supplies,
and trigger interface**



NIF PEPC Modulator: Stalk Impedance

  

Initial Stalk Design:

Top: V_{load} @ 5kV/div (resistive load)


Btm: V_{drain} @ 200V/div

Corrected Stalk Design:

Btm: V_{load} @ 5kV/div

Initially did not meet risetime requirement into load. This was due to stalk impedance being too high resulting in multiple reflections within modulator which slow down output risetime. MOSFET switching transitions are fast enough to meet requirements.

KEK ATF Adder Conceptual Layout

 

Prototype Components - MOSFET Drive Board

Master Trigger Circuit


Trigger Distribution
Traces

Capacitor Array -
Surface Mount Ceramics


MOSFET Drivers

MOSFETs

Charge Circuit

 

Partial Assembly of Prototype

 


Finished Prototype

Output
connectors


Trigger
Cables

 Houses
trigger
distribution,
power
supplies, etc




KEK ATF Modulator Output Characteristics

 Simultaneous bi-polar outputs: 50 Ω load on each end



Negative Output,
-9.6 kV Flattop

 

Positive Output,
+9.6 kV Flattop


Areas of Advanced Development for the DR Application

- Decrease output pulse length
 - Improve MOSFET switching
 - Decrease propagation delays
- Improve pulse-to-pulse stability
 - Reset adder core / stabilize hysteresis
 - Recharge energy storage caps
- Address transmission line effects
 - Degradation of rise/fall time
- Cooling
 - $P_{\text{peak}} \sim 8 \text{ MW}$, $\langle P_{\text{burst}} \rangle \sim 100 \text{ kW}$, $\langle P \rangle \sim 0.5 \text{ kW}$

Output Pulse Length Reduction


- Propagation delay through IC drivers typically 10 ns (or greater)
 - Discrete component driver
 - Advanced topology, e.g. Cascode
- Overcome package inductance:
 $L_G \sim L_S \sim 5 \text{ nH}$, $di/dt \sim 10^{10} \text{ A/s}$
 - Higher voltage driver
 - Hybrid packaging

Discrete Driver

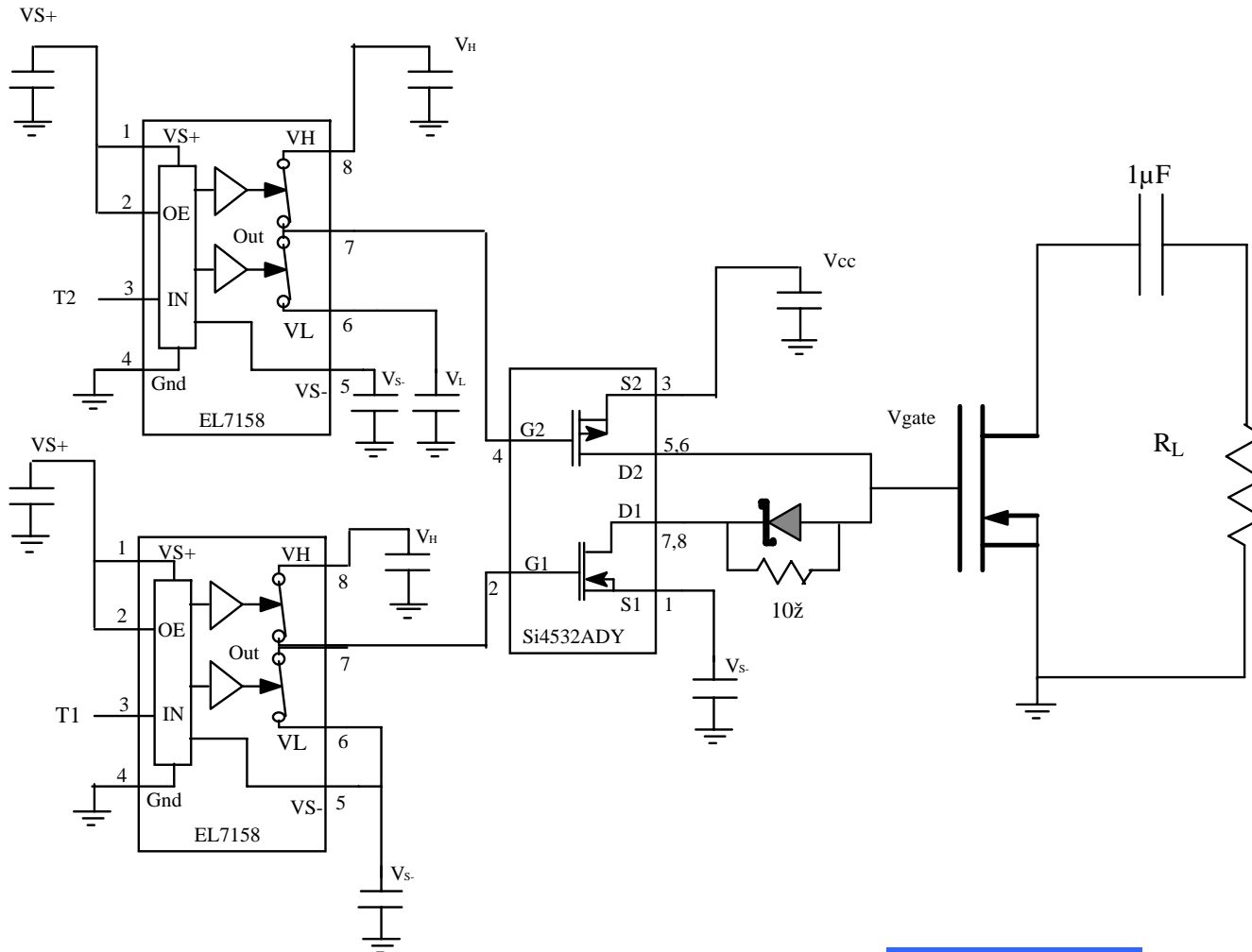


Test Results: 50 Pulse Burst @ 3 MHz, 10 Ω Load, 500 V Charge


2 pulses
from
burst

 


1st
pulse of
burst

 



10th
pulse of
burst

 

40th
pulse of
burst

 


Cascode Driver

 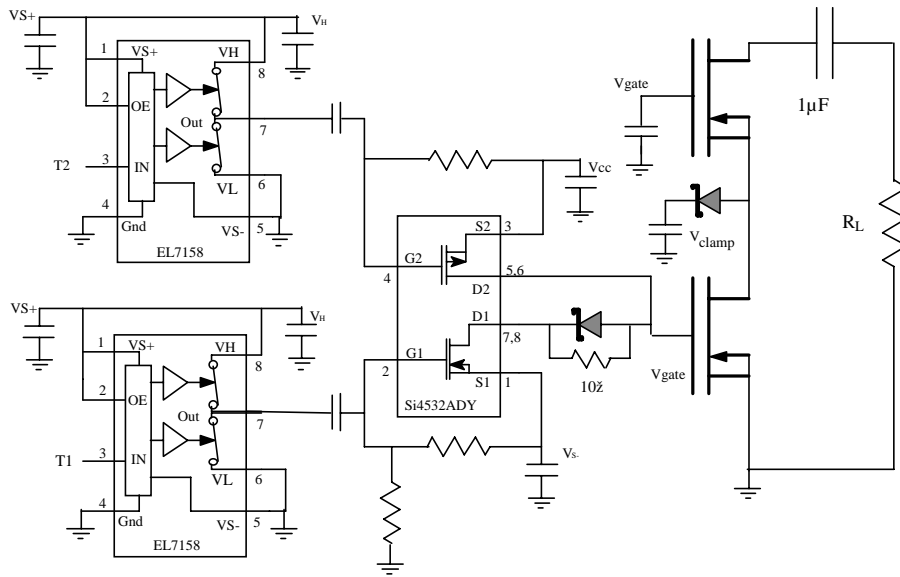

Pulse-to-Pulse Stability

- LLNL adders typically reset/recharge between bursts
 - 3000 pulses, ~ 3 ns $\rightarrow 9 \mu$ s
 - ~ 1 kV $\rightarrow \sim 10^{-2}$ V•s (Alt: use remnant flux)
 - ~ 400 A $\rightarrow \sim 4$ mC
- First Point Scientific adders reset/recharge between pulses
 - Minimum voltage on load $\propto 1/D.F.$

Transmission Line Effects

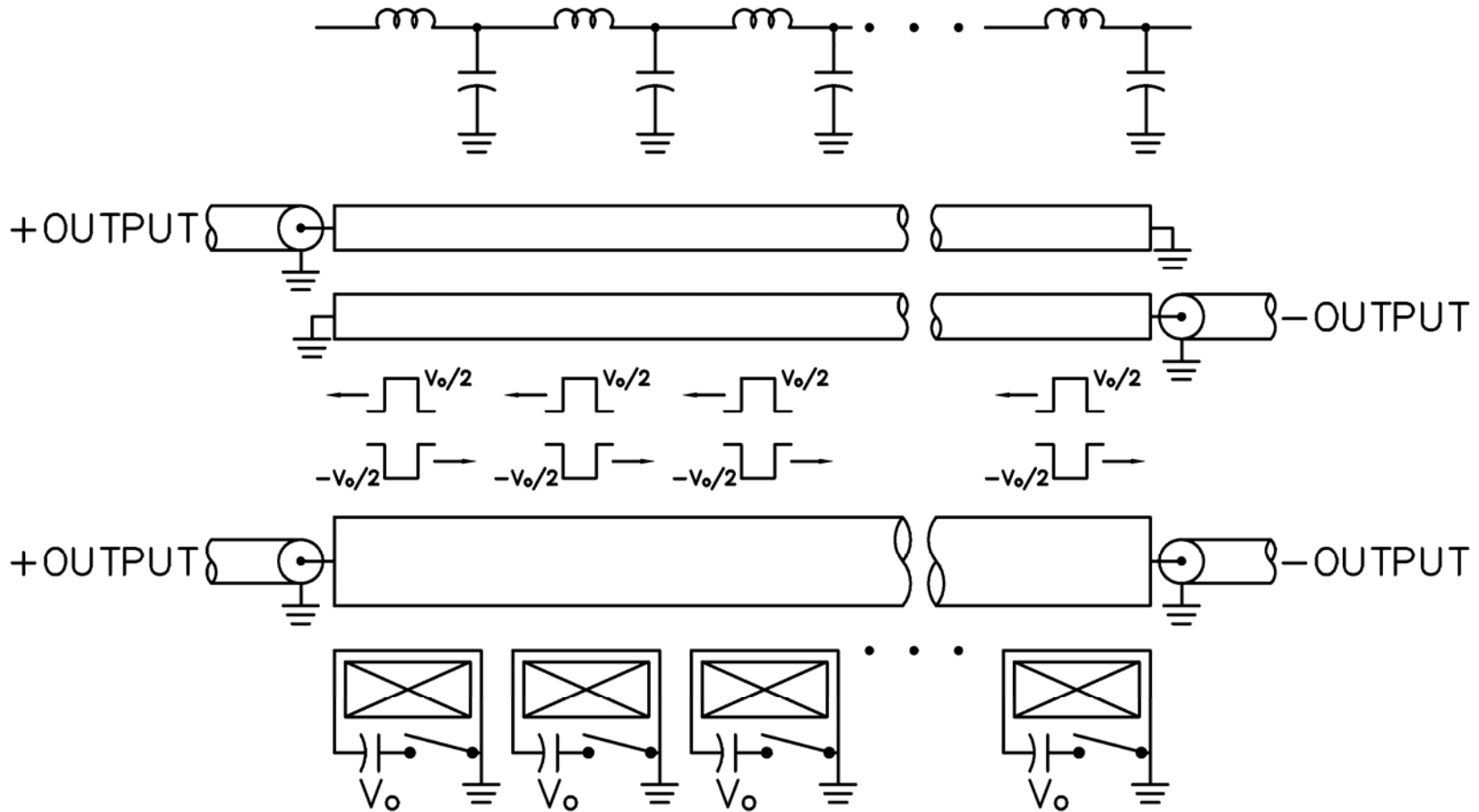

Summary

- SLAC/LLNL program is designed to demonstrate *Full System Architecture* for a High Availability Damping Ring Kicker System
- Inductive adder modulator topology
 - Inherently redundant
 - Mature technology
 - Demonstrated over wide range of parameters
- Focus of SLAC/LLNL program is advanced development areas required to meet ILC parameters
 - Short-pulse prototype
 - Timing, calibration, and controls
 - System testing