



The design of the TimePix chip


Xavier Llopert, CERN

MPI-Munich, October 2006



From Medipix to Timepix

 - ◆ A novel approach for the readout of a TPC at the future linear collider is to use a CMOS pixel detector combined with some kind of gas gain grid
- ◆ Using a *naked* photon counting chip Medipix2 coupled to GEMs or Micromegas demonstrated the feasibility of such approach





Motivation


- ◆ These experiments (by NIKHEF/Saclay, Freiburg 2004/2005) demonstrated that single electrons could be detected using a *naked* Medipix2 chip \Rightarrow 2D
- ◆ Did not provide information on the arrival time of the electron in the sensitive gas volume \Rightarrow 3D (position + time) !!!
- ◆ To further exploit this approach the Medipix2 is being redesigned to incorporate a time stamp with a tunable resolution of 100 to 10ns.
- ◆ Requirements:
 - ◆ Keep Timepix as similar as possible to Medipix2 in order to benefit from large prior effort in R/O hardware and software
 - ◆ Avoid major changes in pixel and/or readout logic - risk of chip failure due to poor mixed mode modelling
 - ◆ Eliminate 2nd threshold
 - ◆ Add possibility of programming pixel by pixel arrival time or TOT information
- ◆ This modification is supported by the JRA2/EUDET Collaboration (www.eudet.org)



Where we come from (Mpix2MXR20 Schematic)

Pixel Configuration Bits

Maskbit	Masks pixel
TestBit	Enables TestPulse
BLO	Low Threshold - B0
BL1	Low Threshold - B1
BL2	Low Threshold - B2
BH0	High Threshold - B0
BH1	High Threshold - B1
BH2	High Threshold - B2

 




Where we go... (Timepix Schematic)

Pixel Configuration Bits


Maskbit	Masks pixel
TestBit	Enables TestPulse
BLO	Low Threshold - B0
BL1	Low Threshold - B1
BL2	Low Threshold - B2
BL3	Low Threshold - B3
P0	Mode Selection - P0
P1	Mode Selection - P1

 



Medipix → Timepix: Analog side changes

 
- ◆ Changes in Preamp:
 - ◆ Added cascode to preamp
- ◆ Changes in the discriminator:
 - ◆ Only 1 discriminator
 - ◆ 4-bit threshold equalization
 - ◆ Polarity control
 - ◆ Added hysteresis







Medipix → Timepix: Preamplifier change

- ◆ Added cascode (8-bit DAC controlled):
 - ◆ Gain \uparrow ($\sim 18\text{mV/Ke}^-$) keeping V_{outrms} noise $\approx \text{cte} \rightarrow \text{SNR} \uparrow$
 - ◆ Expected ENC $\approx 75\text{e}^-$
 - ◆ Expected Linearity: 0.6 to 1.5 Volts $\rightarrow \approx 50\text{Ke}^-$ linear range
 - ◆ Expected Mismatch: $\sigma_{vt} \approx 2.11\text{mV} \rightarrow \sigma_{vt} \approx 117\text{e}^-$

 



  Medipix → Timepix: Preamp Out vs Ikrum DAC





- ◆ 18.75 Ke input charge
- ◆ Ikrum DAC set: 5, 10, 20 and 40
- ◆ Direct measurement on the Timepix test output pads

- ◆ 18.75 Ke input charge
- ◆ Ikrum current set: 1.7, 3.4, 6.8, 13.6 nA



Medipix → Timepix: Gain Linearity

  - ◆ Expected gain linearity up to $\sim 50\text{Ke}^-$
- ◆ $>50\text{Ke}^-$ the Preamp output saturates




Measurement: ΔQ_{in} and ΔI_{krum}




Medipix → Timepix: Preamp Out vs Preamp DAC

 - ◆ Gain (ENC noise) depends on the preamp current
- ◆ Tunable peaking time: ~90ns to 400ns → check Time-walk!





 
TestPulse on 1 pixel (Medipix Mode) Ikrum=5






Medipix → Timepix: Discriminator changes

 - ◆ Added hysteresis (8-bit DAC controlled) in discriminator:
 - ◆ ~ $200e^-$ lower threshold and no glitches at the disc output
 - ◆ It can be turned off
- ◆ Polarity selection on the discriminator:
 - ◆ Hysteresis possible
 - ◆ Optimization of the zero crossing design
- ◆ 4-bit threshold adjustment:
 - ◆ Expected Threshold dispersion after adjustment ~ $25e^-$






Medipix → Timepix: Discriminator Output

 




Medipix → Timepix: Time walk Simulation-Measurement

 - Measured timewalk with the default DAC values
- Possible offline correction combined with TOT measurement can bring timewalk < Ref_Clk period





Simulation

 

Measurement: ΔThr



  Medipix → Timepix: TOT vs Ikrum (simulation)





◆ TOT Linearity > 200 Ke^-



Medipix → Timepix: TOT vs Ikrum (measurement)

 
 
- ◆ TOT gain is a function of Ikrum DAC setting
- ◆ Ref_Clk=71.1MHz





Timepix equalization (I)

  - ◆ Equalization using the noise as trigger and Medipix Mode ($P0=P1=0$)
- ◆ The measured DNL of the 4-bit DAC is $< 1\text{THL DAC}$ → Interpolation in the equalization can be used





Analog pixel summary


	Simulated	Measured
Amplifier Gain	$\sim 18 \text{mV/Ke}^-$	$\sim 16.06 \text{mV/Ke}^-$
Peaking Time (Δ Preamp)	90ns...400ns	90ns...400ns
Pixel noise	$\sim 75 e^-_{\text{rms}}$	$\sim 98 e^-_{\text{rms}}$
Threshold dispersion	$\sim 170 e^-$	$\sim 225 e^-$
Adjusted Threshold dispersion	$\sim 25 e^-$	$\sim 38 e^-$ (not optimized)
Voltage linear range	0 to 50 Ke $^-$ (< 2%)	Measured up to 20Ke $^-$
TOT linear range	>200Ke $^-$	Measured up to 50Ke $^-$
Time Walk	$\sim 25 \text{ns}$ (2Qth to ∞)	$\sim 60 \text{ns}$ (with default DACs)
TOTgain	$\sim 55 \text{ns/Ke}^-$ ($I_{\text{krum}}=5 \text{nA}$)	52.7ns/Ke^- ($I_{\text{krum}_{\text{DAC}}}=20$)
Analog Pixel consumption (Max)	$2.9 \mu\text{A} \times 2.2 \text{V} = 6.38 \mu\text{W}$ (30% less than Mpix2MXR20)	

- ◆ Maximum possible Qin injected via Testpulse is $\sim 50 \text{Ke}^-$





Medipix → Timepix: Digital side changes

 - ◆ Added time reference (Ref_Clk)
- ◆ Selectable operation modes (P0 and P1)
- ◆ TSL (Timepix synchronization Logic)
- ◆ Pixel-by-pixel synchronized Shutter





  
Medipix → Timepix: Added Time reference (I)



- ◆ Column length= $55 \times 256 = 14080 \mu\text{m}$
- ◆ $W=0.4 \mu\text{m}, T=0.54 \mu\text{m}, H=0.8 \mu\text{m}$
- ◆ $R \approx 2.8 \text{ k}\Omega$
- ◆ $C_{tot} \leq 2 \text{ pF}$
- ◆ Parasitic cap negligible at $D > 3 \mu\text{m}$




 Medipix → Timepix: Added Time reference (II)



N buffer per column:

 
- ◆ Min size buffer \Rightarrow inverter per pixel
- ◆ No differential signals needed
- ◆ Power uniformly distributed over clock period



- ◆ $N=256, f=100\text{MHz}$
- ◆ Propagation delay = $\sim 50\text{ns}$ ($\sim 195\text{ps}/\text{inv}$)
- ◆ Simulation takes care of parasitic capacitances and top-down resistive power lines.



 Medipix → Timepix: Expected digital power dissipation



- ◆ $P_{Vdd} = V^2 \cdot f \cdot C_{tot}$
- ◆ Simulation @ $V_{dd} = 2.2\text{V}$
but digital part could work to 1.8V (33% less power)



Medipix → Timepix: TSL


- ◆ Use of 3-bit High threshold adjustment bits for : 4th equalization bit and P0, P1.
- ◆ Each pixel can be configured independently in 5 different modes.
- ◆ This logic needs 128 Trts (Mpix2MXR20 had 92 Trts)

Mask	P1	P0	Mode
0	0	0	Masked
0	0	1	Masked
0	1	0	Masked
0	1	1	Masked
1	0	0	Medipix
1	0	1	TOT
1	1	0	Timepix-1hit
1	1	1	Timepix




Timepix Synchronization Logic (TSL)

- ◆ Hit is synchronized with Ref_Clk and Shutter generating the signal to the counter and internal Shutter depending on P0, P1 and Mask bits.
- ◆ Power consumption only when Hit is present
- ◆ TSL Core is divided in 2 blocks: Core1 used for the Timepix and TOT modes and Core2 used for Medipix mode.
- ◆ Core blocks have been designed using an asynchronous network with S-R Flip-flops with race-free state assignment

 




TSL Core1 Asynchronous design

 


◆ TSL desired time diagrams

 



◆ State diagram



TSL Core Asynchronous design (II)

 



◆ State diagram

  

◆ Reduced State diagram



TSL Core Asynchronous design (III)

 
 


- ♦ Reduced State diagram with initialization

- ♦ Implementation with SR flip-flops (62 trts)




TSL Core2 Asynchronous design

  


- ◆ TSL desired time diagrams
- ◆ Implementation using gates (20 trts) since inputs are race-free "by design"



Timepix Mode (P0=1, P1=1)

 


10MHz

 


100MHz



TOT Mode (P0=1, P1=0)

 


10MHz

 


100MHz



Medipix Mode ($P_0=0, P_1=0$)

 


10MHz

 

100MHz




Internal Shutter control

 

- ◆ Internal Shutter is always synchronous to the clock to avoid glitches
- ◆ Counter starts counting if a hit is present when shutter starts
- ◆ Shutter closing happens with a maximum delay of 1Tclk if a hit is present when shutter closes



Digital power consumption

 


- ◆ Reduce digital power of the TSL cores → No power consumption in stand-by (no hit)
- ◆ In stand-by the only digital consumption is the buffering of the Ref_Clk
- ◆ Controlled by design of the core1 asynchronous network.





Pixel measurements

 - ◆ From the 2 test pixels [120:121,0] one can measure the preampOut, discOut, internal Ref_Clk and the counter clock
- ◆ State Machine of the counter Modes (P0, P1) work as expected
- ◆ No visible coupling of the Ref_Clk signal into the analog signals (preampOut and discOut)






Timepix Layout status

  



Timepix chip architecture

 - Chip architecture almost identical to Mpix2MXR20
 - M0=M1=1 and Shutter ON → FClock used as Ref_Clk
- 256x256 55 μ m square pixels
- Analog Power → 440mW
- Digital Power (Ref_Clk=50MHz) → 220mW
- Serial readout (@100MHz) → 9.17 ms
- Parallel readout (@100MHz) → 287 μ s
- > 36M Transistors






Periphery Verilog Simulations

- ◆ This simulation tests 1 row of pixels and the full chip control logic
- ◆ Tested with normal and corner ($\pm 3\sigma$) parameters successfully
- ◆ Pixel control logic is initialized after a set mask command
- ◆ M0=1 and M1=1 when counting will enable the clock distribution to the pixel matrix

M0	M1	Enable_IN	Shutter	Reset	P_S	I/O	FClock num (per chip)	Operation
X	X	X	X	0	X	I	X	General reset of the chip
1	1	X	0	1	X	X	X	Counting
0	0	0	1	1	0	I/O	917768	Serial Readout Matrix (Slow Reset Matrix)
0	0	0	1	1	1	I/O	28688	Parallel Readout Matrix (Fast Reset Matrix)
0	1	0	1	1	X	I	917768	Set Matrix
1	0	0	1	1	X	I/O	264	Write/Read FSR (DACs and CTPR)




Single chip Verilog simulation

 



Counting Modes (Mask, P0 and P1)

 

- ⇐ Pixel Masked P0=X, P1=X and Mask=1
- ⇐ Tpix-1h mode P0=0, P1=1 and Mask=0
- ⇐ Mpix2 mode P0=0, P1=0 and Mask=0
- ⇐ Tpix mode P0=1, P1=1 and Mask=0
- ⇐ CCD mode P0=1, P1=0 and Mask=0



Medipix2 vs Timepix

	Medipix2	Timepix
Physical dimensions	=	=
IO PADs	=	=
Charge collection	e^- , h^+	e^- , h^+
Pixel functionality	PhotonCounting	PhotonCounting, TOT, Timepix
Amplifier Gain	$\sim 10\text{mV}/\text{Ke}^-$	$\sim 18\text{mV}/\text{Ke}^-$
Noise	$\sim 110e^-$	$\sim 75e^-$
Linearity	Up to 100Ke^-	Up to 50Ke^-
Thresholds	2 (3+3 bits adj)	1 (4bits adj)
σ equalized	$\sim 100e^-$	$\sim 25e^-$
Minimum Threshold	$\sim 900e^-$ (measured)	$\sim 500e^-$ (expected)*
Counter Depth/Overflow	14-bits/Yes	14-bits/Yes
Max Analog power	$10\mu\text{W}/\text{pix}$ $300\text{mA}/\text{chip}$	$6.5\mu\text{W}/\text{pix}$ $190\text{mA}/\text{chip}$
Static Digital Power	none	$200\text{mA}@100\text{MHz}$
Readout	Serial/Parallel	Serial/Parallel
Readout compatibility	100%	95% (Clock active when shutter ON)



Summary & Conclusions

- ◆ Timepix is a modification of the Medipix chip
- ◆ Improvements in Gain and threshold equalization -> expected lower threshold ($\sim 900e^- \rightarrow \sim 600e^-$)
- ◆ Pixel operation mode is selectable for each pixel
- ◆ TimeStamp reference (Ref_Clk) generated by a common clock distributed all over the chip
- ◆ Timepix time line:
 - ◆ Design: 6 months (January06-June06)
 - ◆ Fabrication: 2 months (July06-August06)
 - ◆ Testing: 1 months so far (mid September06-?)